

# Digital System Design

---

## **Combinational Circuit design and Simulation Using Gate**

# Objectives

---

## Topics introduced in this chapter:

- **Draw a timing diagram for a combinational circuit with gate delays.**
- **Define static 0-and 1-hazards and dynamic hazard. Given a combinational circuit, find all of the static 0-and 1-hazards. For each hazard,specify the order in which the gate outputs must switch in order for the hazard to actually produce a false output.**
- **Given switching function, realize it using a two-level circuit which is free of static and dynamic hazards (for single input variable changes).**
- **Design a multiple-output NAND or NOR circuit using gates with limited fan-in.**
- **Explain the operation of a logic simulator that uses four-valued logic.**
- **Test and debug a logic circuit design using a simulator.**

## 8.2 Design of Circuits with Limited Gate Fan-in

Example: Realize  $f(a,b,c,d) = \sum m(0,3,4,5,8,9,10,14,15)$  using 3-input NOR gate


map of  $f$ :

$cd \backslash ab$	00	01	11	10
00	1	1	0	1
01	0	1	0	1
11	1	0	1	0
10	0	0	1	1

$$f' = a'b'c'd + ab'cd + abc' + a'bc + a'cd'$$
 
## 8.2 Design of Circuits with Limited Gate Fan-in

$$f' = b'd(a'c') + a'c(b + d') + abc'$$
$$f = [b + d' + (a + c)(a' + c')][a + c' + b'd][a' + b' + c']$$



## 8.2 Design of Circuits with Limited Gate Fan-in


Example: Realize the functions given in Figure 8-2,  
using only 2-input NAND gates and inverters.

If we minimize each function separately, the result is


$$f_1 = b'c' + ab' + a'b$$

$$f_2 = b'c' + bc + a'b$$


$$f_3 = a'b'c + ab + bc'$$

 

$$f_1 = \Sigma m(0, 2, 3, 4, 5)$$

 

$$f_2 = \Sigma m(0, 2, 3, 4, 7)$$

 

$$f_3 = \Sigma m(1, 2, 6, 7)$$

Figure 8-2

## 8.2 Design of Circuits with Limited Gate Fan-in

 


Figure 8-3: Realization of Figure 8-2

$$f_1 = b'(\underline{a+c'}) + \underline{a'b}$$

$$f_2 = b(a'+c) + \underline{b'c'}$$



$$f_3 = a'b'c + b(\underline{a+c'})$$

$$f_2 = (b'+c) \bullet (b+c') + \underline{a'b}$$

$$a'b'c = a'(b'c) = a'(b+c')'$$

## 8.3 Gate Delays and Timing Diagrams



### Propagation Delay in an Inverter

  

- ④ Output of logic gates take some time to change value (propagation delay)
- ④ The propagation delay may be different for input  $0 \rightarrow 1$ , and  $1 \rightarrow 0$

## 8.3 Gate Delays and Timing Diagrams

  
### Ex: Timing Diagram for AND-NOR Circuit





## 8.3 Gate Delays and Timing Diagrams
 
### Timing Diagram for Circuit with Delay




- ④ The input  $X$  consists of two pulses:
- ④ The first of which is 2 microseconds ( $2 \times 10^{-6}$  second) wide and the second is 3 microseconds wide.

 
## 8.4 Hazards in Combinational Logic

---

- ④ **Static 1-hazard**: a circuit output may momentarily go to 0 when it should remain a constant 1.
- ④ **Static 0-hazard**: a circuit output may momentarily go to 1 when it should remain a constant 0.
- ④ **Dynamic hazard**: output change 3 or more times when the output changes from 0 to 1 (1 to 0)



(a) Static 1-hazard

 

(b) Static 0-hazard



(c) Dynamic hazards


Types of Hazards



## Example (1/2)

### ④ Example of 1-hazard: (Fig. 8-8)

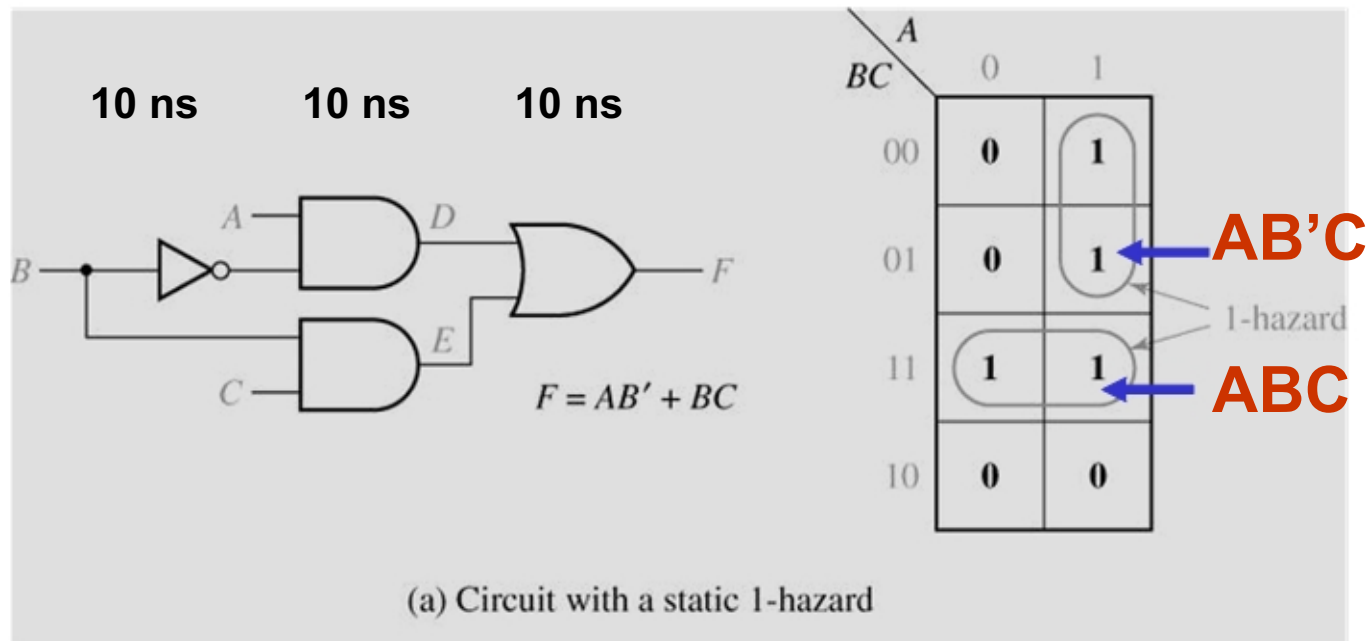1.  $A = C = 1$
2. After  $B$  changes to 0, both  $B$  and  $B'$  are 0 until the propagation delay is elapsed.





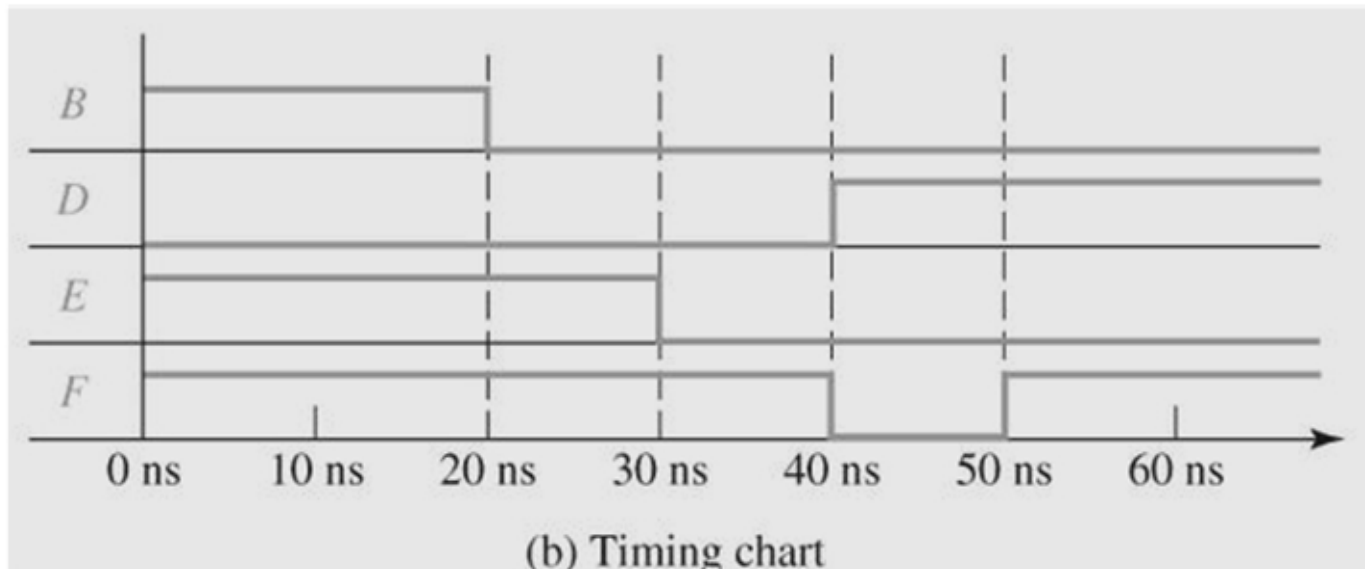
## Example (2/2)


- ④ Check hazard from K-map: No loops cover both minterms  $ABC$  and  $AB'C$ .

↗ When  $A = C = 1$ ,  $B$  changes  $\Rightarrow$  Both terms go momentarily to 0 ↗ Glitch in  $F$ .




## 8.4 Hazards in Combinational Logic

### Detection of a 1-Hazard

 

(a) Circuit with a static 1-hazard

 


(b) Timing chart

## 8.4 Hazards in Combinational Logic

### Hazard in 2-level AND-OR network

1. Write down SOP form.
2. Plot each term on map and loop it.
3. If any two adjacent 1's are not covered by the same loop, a 1-hazard exists.  
For an n-variable map, this transition occurs when one variable changes and the other (n-1) variables are held constant.
4. Solution: Insensitive to change of B: AC keeps on 1 when B changes.

#### Circuit with Hazard Removed

 

BC \ A	0	1
	00	01
00	0	1
01	0	1
11	1	1
10	0	0





## Example (1/3)

1.  $A = 0, B = 1, D = 0, C$  from 0 to 1


⌘ 0-hazard

 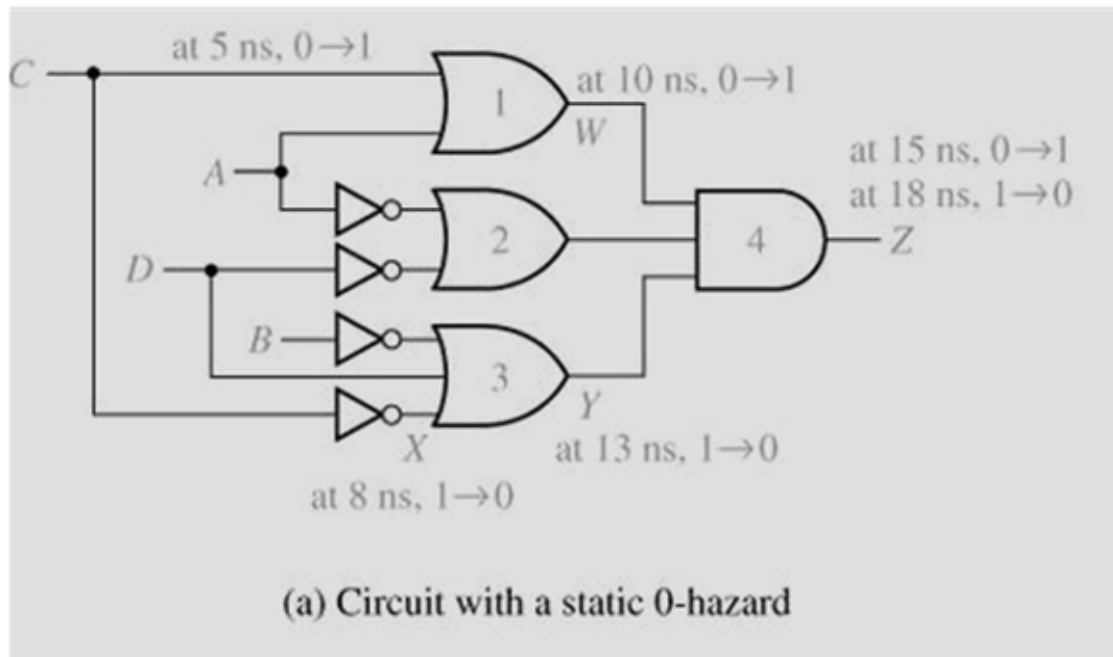2. Delay:      Invert: 3ns      AND/OR: 5ns





## Example (2/3)

 


(c) Timing diagram illustrating 0-hazard of (a)





## Example (3/3)

 


⌘ Add 3 addition loops

$$\underline{\underline{F}} = (A + C)(A' + D')(B' + C' + D)(C + D')(A + B' + D)(A' + B' + C')$$


## 8.4 Hazards in Combinational Logic

### Detection of a Static 0-Hazard


$$F = (A + C)(A' + D')(B' + C' + D)$$

 

(a) Circuit with a static 0-hazard

 


(b) Karnaugh map for circuit of (a)

 

(c) Timing diagram illustrating 0-hazard of (a)

## 8.4 Hazards in Combinational Logic

### Karnaugh Map Removing Hazards

 

$$F = (A + C)(A' + D')(B' + C' + D)(C + D')(A + B' + D)(A' + B' + C')$$



# Simulation of Logic Gates


## ④ Logic circuits are verified by

- { Actually build them
- { Computer simulation


- 1) Computations are performed stage-by-stage (From input)
- 2) Evaluations are performed every time inputs change.
  - { X: value of gate input is unknown Z: open circuit or high-impedance (hi-Z)

## 8.5 Simulation and Testing of Logic Circuit

---

 

(a) Simulation screen showing switches

 

(b) Simulation screen with missing gate input

**Four-valued  
logic values:**

**0,1,X(unknown)  
, Z(hi-Z)**

## 8.5 Simulation and Testing of Logic Circuit

### And and OR Functions for Four-Valued Simulation

x	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X

AND  
Gate


+	0	1	X	Z
0	0	1	1	1
1	1	1	1	1
X	X	1	X	X
Z	X	1	X	X

OR  
Gate

## 8.5 Simulation and Testing of Logic Circuit

### Logic Circuit with Incorrect Output

 Example:  $F = AB(CD' + CD') + A'B'(C + D)$





# **Possible Errors in Your Designs**

- ④ In simulations:
  - ④ Incorrect design
  - ④ Gates connected wrong
  - ④ Wrong input signals to the circuits
- ④ In actual circuits
  - ④ Defective gates
  - ④ Defective connecting wires